

Analog Circuits Design

Electronics Club, IIT Kanpur





Outline

- Op-amp
 - Basics
 - Amplifiers
 - Adder and subtractor
 - Filters
 - Schmidt Trigger
- BJT
 - Inverter
 - CE amplifier





Op-amp

- An ideal op-amp
 - Infinite differential gain
 - Zero common mode gain
 - Infinite input impedance
 - Zero output impedance
 - Infinite bandwidth
- Some non-idealities
 - Finite gain
 - Offset voltage
 - Finite output voltage
 - Finite bandwidth



Op-amp

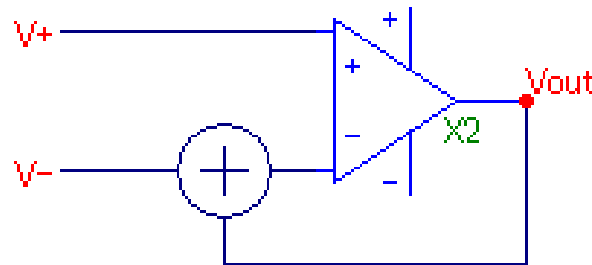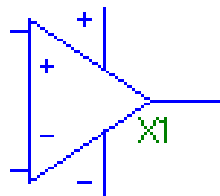
- An almost ideal black box.
- Very high differential gain and input impedance.
- Gain control through negative feedback.
- **Virtual Short**






Op-amp Amplifier

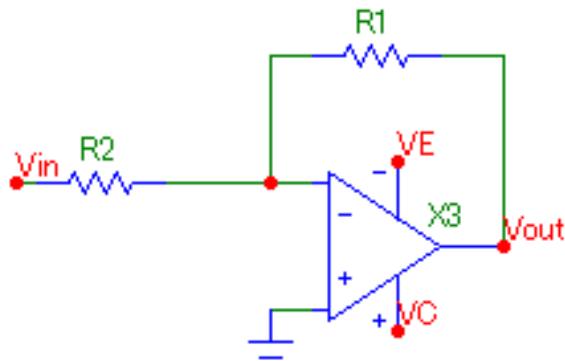- Negative feedback through resistors.
- Inverting amplifier.
- Non-inverting amplifier.
- Buffer


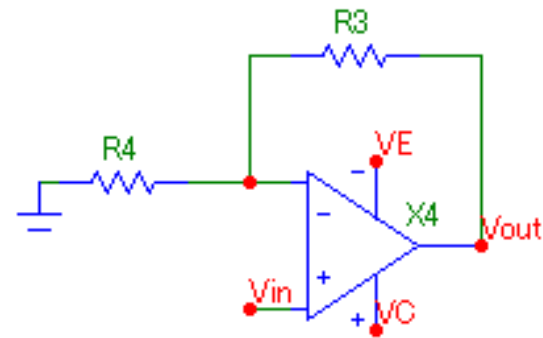
$$\frac{V_{out}}{V_{in}} = -\frac{R1}{R2}$$




$$\frac{V_{out}}{V_{in}} = 1 + \frac{R3}{R4}$$




Op-amp adder

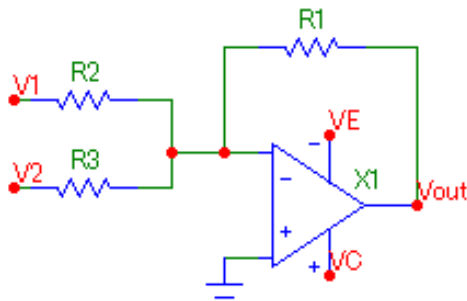- Analysis is similar to an inverting or non-inverting amplifier.


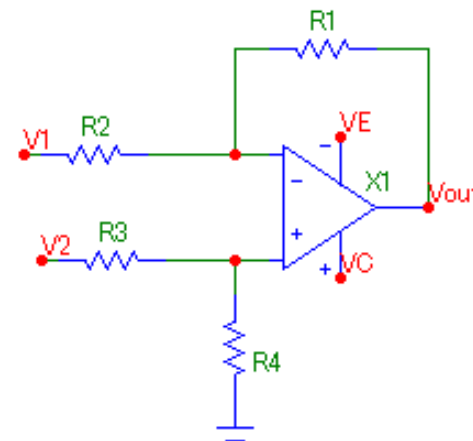
$$V_{out} = -\frac{R_1}{R_2} (V_1 + V_2)$$





$$V_{out} = V_2 \frac{R_4(R_1 + R_2)}{R_2(R_3 + R_4)} - V_1 \frac{R_1}{R_2}$$



Op-amp Filters

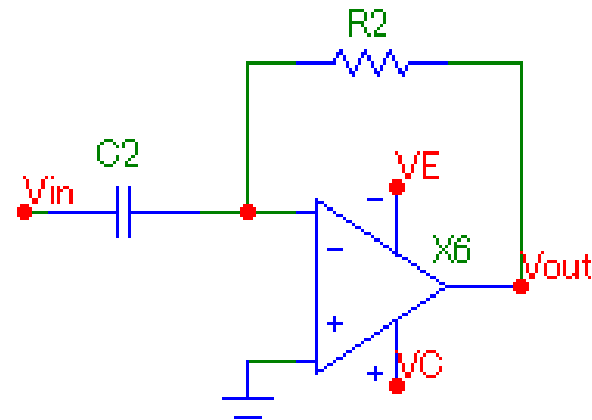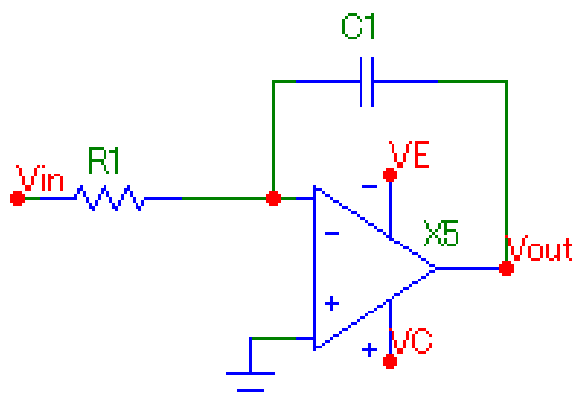
- Filters – Low pass, High pass, and Band pass
- Integrator
- Differentiator





Op-amp


- Positive feedback
- Schmitt trigger

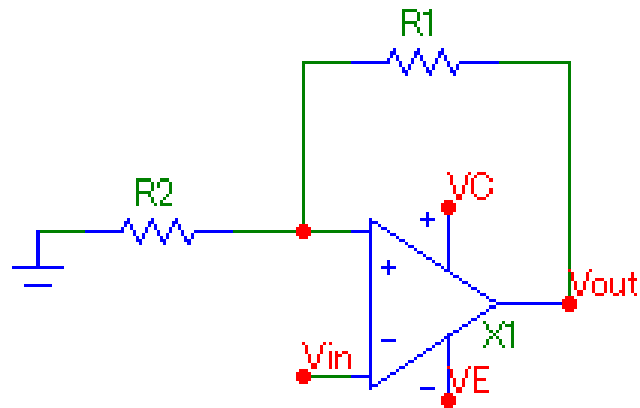



Schmitt trigger multi-vibrator


- Made using a Schmitt trigger

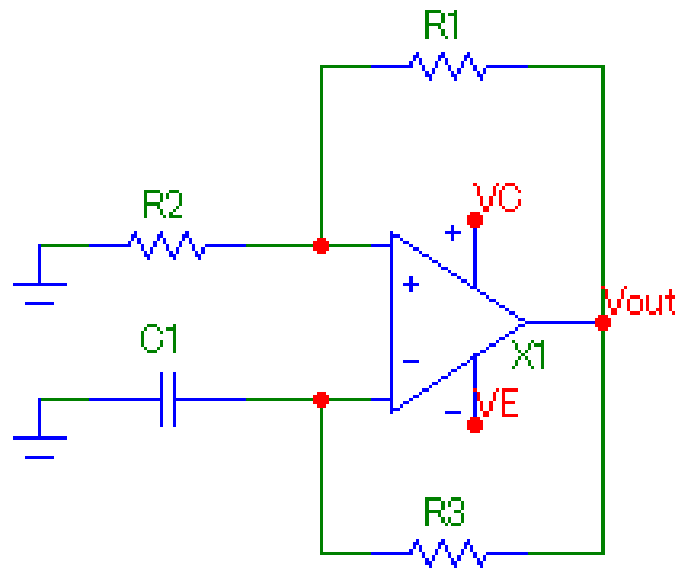



Bipolar Junction Transistor

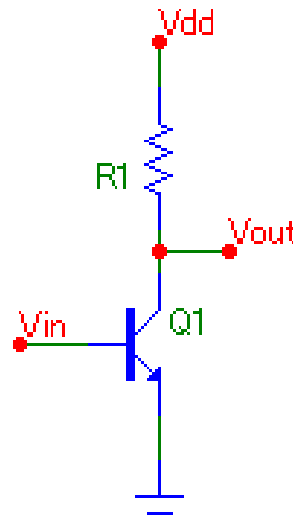- Most basic operation is a switch.
- Can be used to make a simple inverter.
- Also can be used as an amplifier.





Thank You...

Electronics Club
<http://students.iitk.ac.in/eclub/>