

Digital Logic Design using Verilog and FPGA devices Part 1

An Introductory Lecture Series

By

Chirag Sangani

Terminology

- Verilog: A “Hardware Description Language”.
- FPGA: “Field Programmable Gate Array”.
Physically, it is an IC on a circuit board.
- Synthesizer: A tool to convert Verilog code into a useful format (?), analogous to a compiler.

Verilog

- It is NOT a programming language, although its syntax is similar to that of C.
- C describes a “Computer Program” which is a sequence of instructions carried out by the computer processor on an input to give the desired output.


Verilog

- Verilog describes an electronic circuit (for our purposes, the circuit is digital in nature).
- The Verilog code is synthesized (analogous to compiled) to give the circuit logic diagram.
- This circuit can then either be simulated on a computer, or can be fabricated into an actual circuit in the form of an IC.

FPGA

- An FPGA is a device that allows you to implement your synthesized circuit in the real world.
- Physically, it is an IC with a large number of lookup tables and a complicated wire network that can be programmed to work as any desired digital circuit.

Development process

 

Verilog Examples: Repeater

```
module Repeater(  
    input wire A,  
    output wire B);  
  
    assign B = A;  
  
endmodule
```

Verilog Examples: Bus Inverter


```
module BusInverter(  
    input wire [31:0] A,  
    output wire [31:0] B  
);  
  
    assign B = ~A;  
  
endmodule
```

Advanced Example: Seven Segment Decoder

- A seven segment decoder receives a 4-bit unsigned number as an input and gives an output in a particular manner.
- This output can be used to drive the segments of a seven-segment display.

Advanced Example: Seven Segment Decoder

I3	I2	I1	I0	A	B	C	D	E	F	G
0	0	0	0	0	0	0	0	0	0	1
0	0	0	1	1	0	0	1	1	1	1
0	0	1	0	0	0	1	0	0	1	0
0	0	1	1	0	0	0	0	1	1	0
0	1	0	0	1	0	0	1	1	0	0
0	1	0	1	0	1	0	0	1	0	0
0	1	1	0	0	1	0	0	0	0	0
0	1	1	1	0	0	0	1	1	1	1
1	0	0	0	0	0	0	0	0	0	0
1	0	0	1	0	0	0	0	1	0	0
1	0	1	0	0	0	0	1	0	0	0
1	0	1	1	1	1	0	0	0	0	0
1	1	0	0	0	1	1	0	0	0	1
1	1	0	1	1	0	0	0	0	1	0
1	1	1	0	0	1	1	0	0	0	0
1	1	1	1	0	1	1	1	0	0	0

 

Advanced Example: Seven Segment Decoder

```
module SevenSegmentDisplay(  
    input wire [3:0] inp,  
    output wire[6:0] out  
);  
  
assign out[0] = ~inp[3] & ~inp[2] & ~inp[1] &  
inp[0]  
| ~inp[3] & inp[2] & ~inp[1] & ~inp[0]  
| inp[3] & ~inp[2] & inp[1] & inp[0]  
| inp[3] & inp[2] & ~inp[1] & inp[0];  
  
endmodule
```

Introducing the always Block

- The always block allows for the implementation of sequential and combinatorial circuits.
- It allows to shift our programming focus from being logic-based to behavior-based.

Anatomy of an always block

```
always @(#sensitivity list#)
begin
    #actions#
end
```

The Sensitivity List

```
// Run continuously.  
always
```

```
// Run when any variable changes its value.  
always @(*)
```

```
// Run when the variables `a' or `b' change their  
value.  
always @(a,b)
```

```
// Run when a positive edge is detected on CLK.  
always @(posedge CLK)
```

Example: Counter

```
module Counter(  
    input wire CLK,  
    output reg [31:0] OUT  
);  
  
initial  
    OUT <= 0;  
  
always @(posedge CLK)  
    OUT <= OUT + 1;  
  
endmodule
```


Points to Note

- Output is reg instead of wire.
Why?
- The operator used is <= instead of =.
Why?
- An initial block is added. What is it and why?

```
module Counter(  
    input wire CLK,  
    output reg [31:0] OUT  
);  
  
initial  
    OUT <= 0;  
  
always @(posedge CLK)  
    OUT <= OUT + 1;  
  
endmodule
```

Revisiting the Seven Segment Decoder
 
```
module SevenSegmentDecoder2(  
    input wire [3:0] inp,  
    output reg [6:0] out);  
  
initial  
    out <= 7'b0;  
  
always @(*)  
begin  
    case (inp)  
        4'b0001: out <= 7'b0000110;  
        default: out <= 7'b0111111;  
    endcase  
  
end  
  
endmodule
```



References

- R. Haskell, D. Hanna: “Introduction to Digital Design Using Digilent FPGA Boards – Block Diagram / Verilog Examples”; available at [http://www.digilentinc.com/Data/Textbooks/Intro to Digital Design-Digilent-Verilog Online.pdf](http://www.digilentinc.com/Data/Textbooks/Intro%20to%20Digital%20Design-Digilent-Verilog%20Online.pdf)
- C. Sangani, A. Kasina: “Digital Design Using Verilog and FPGAs: An Experiment Manual”; available at <http://www.chiragsangani.com/projects/electronics/FPGADesignManual>