


Analog Circuit Design

AVI SINGH




Amplifier

What is an amplifier?

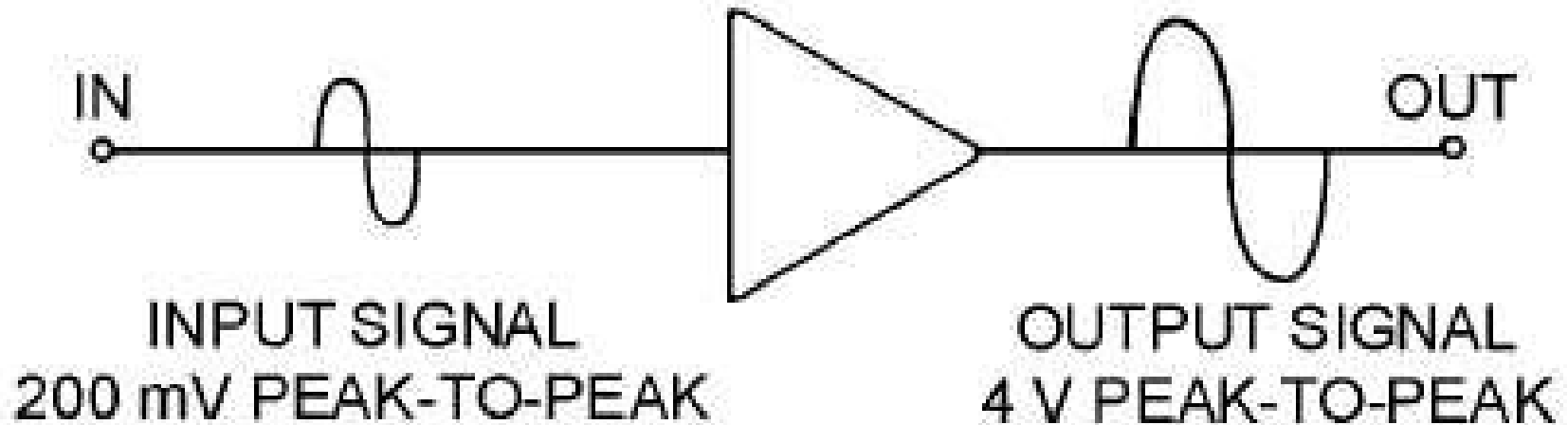

Necessary Conditions

There is a “power gain”.

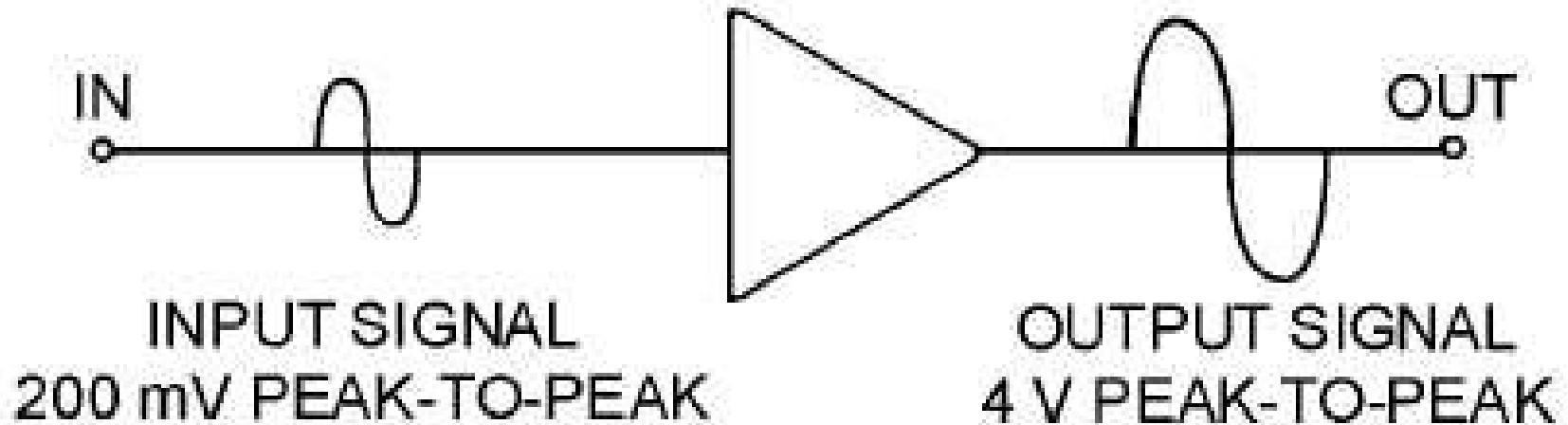


Voltage Amplifier

Input and output: both are voltages

LHS: Input Terminal




RHS: Output Terminal

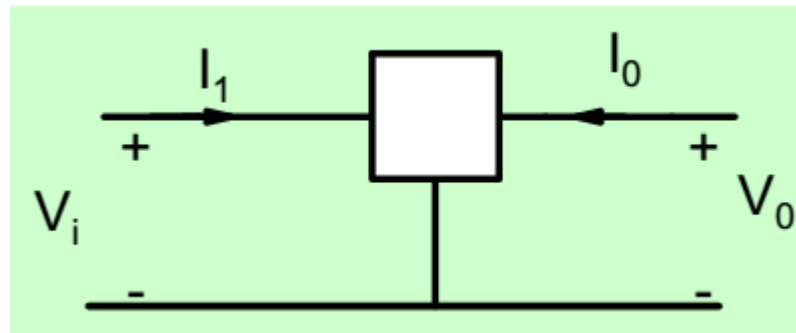The bottom wire is similar to a 'common ground'



An equivalent Circuit

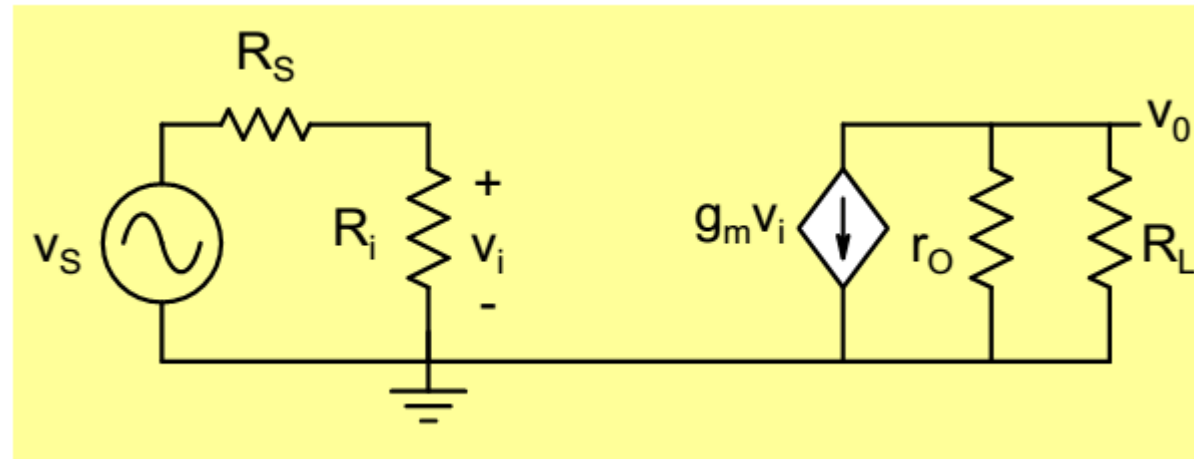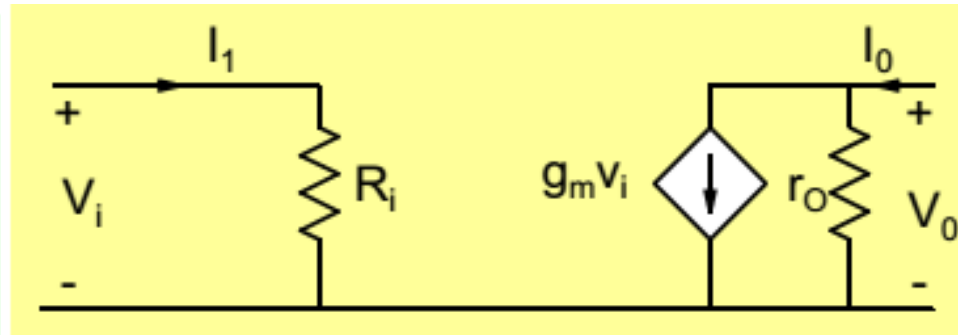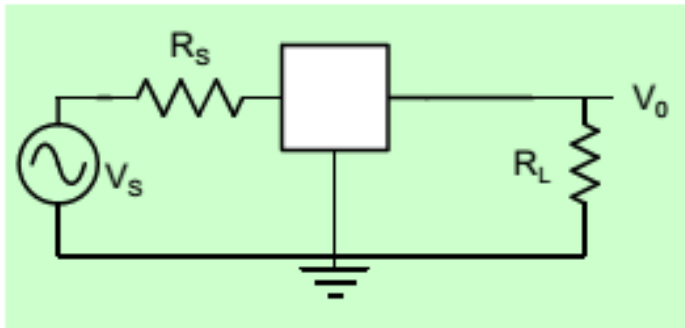Note: There is a voltage-dependent current source in the circuit.





How do we build an amplifier?

Amplifiers cannot be built simply using resistors, capacitors or inductors alone.

You need external power source also (for the power gain).

Some 'simple' amplifier designs

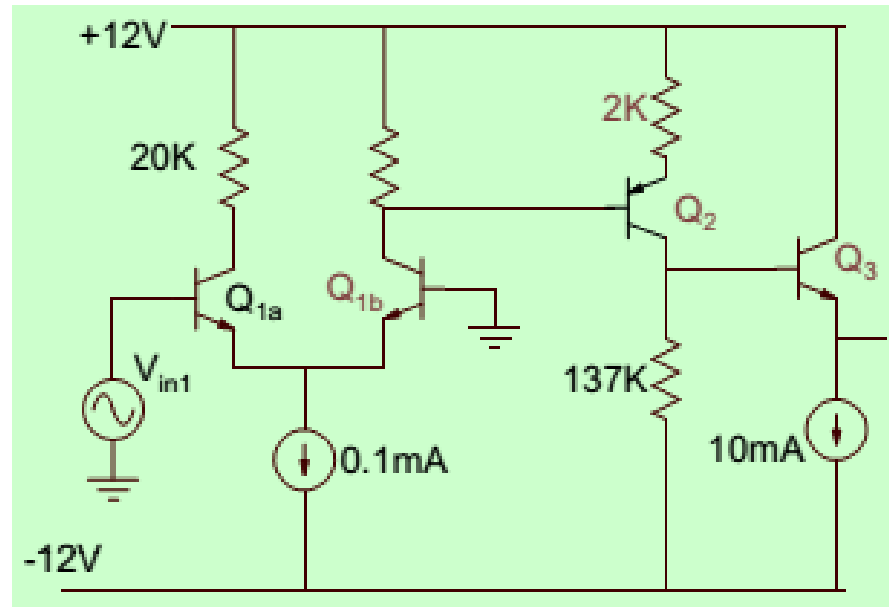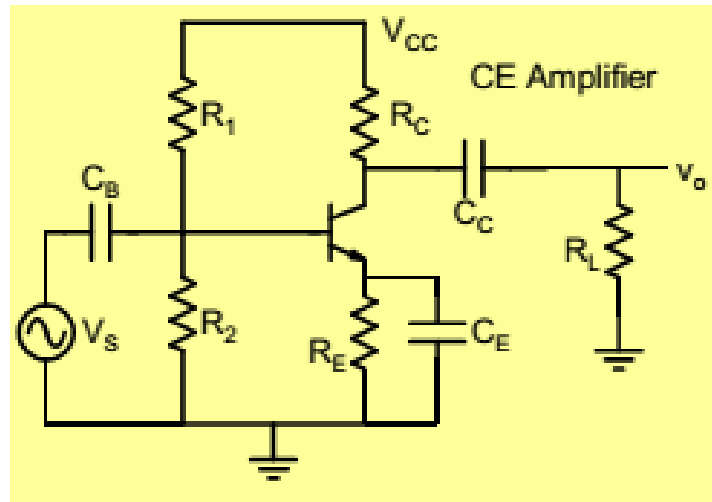It is not possible for everyone to design their own amplifiers without



So, how do we proceed?

Our dilemma: Amplifiers already might not satisfy all our specific requirements, while it is very difficult to design a good amplifier from scratch.


The answer: A Semi-Custom Approach

We use some amplifiers that have been already built, and customize them according to our own requirements.

An Example of such an amplifier that we can customize according to our needs: An Operational Amplifier

Difference Amplifiers

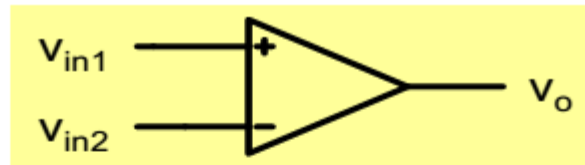They are insensitive to what is common between two signals, and sensitive to what is different:



$$v_{id} = v_{in1} - v_{in2}$$

$$v_{ic} = \frac{v_{in1} + v_{in2}}{2}$$

$$v_o = A_d v_{id} + A_{cm} v_{ic}$$

A_d : Differential mode gain

A_{cm} : Common mode gain


$$A_d \gg A_{cm}$$

$$\text{Common Mode Rejection Ratio: } CMRR = \frac{A_d}{A_{cm}}$$



An Operational Amplifier(Op-Amp)

A special type of difference amplifier

Very high common mode rejection ratio.


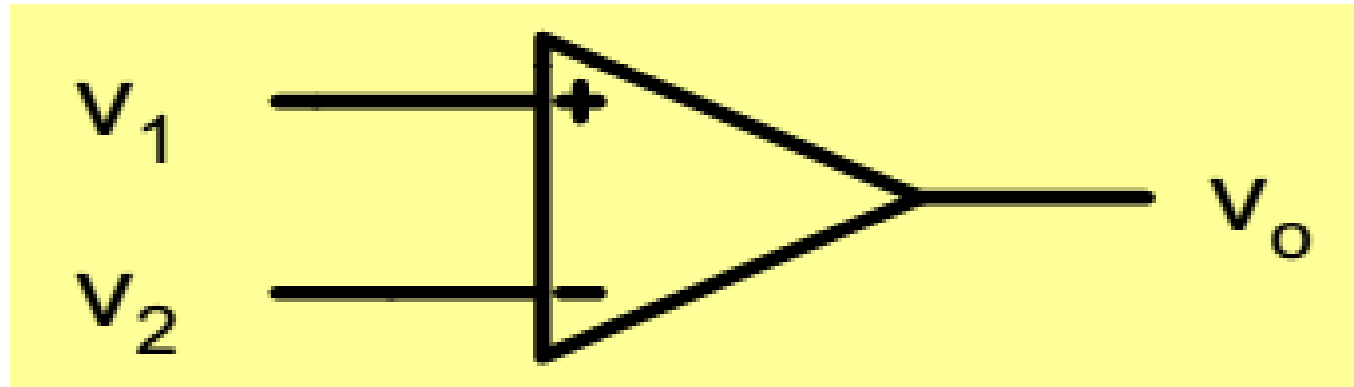


Equivalent Circuit of an Op-Amp

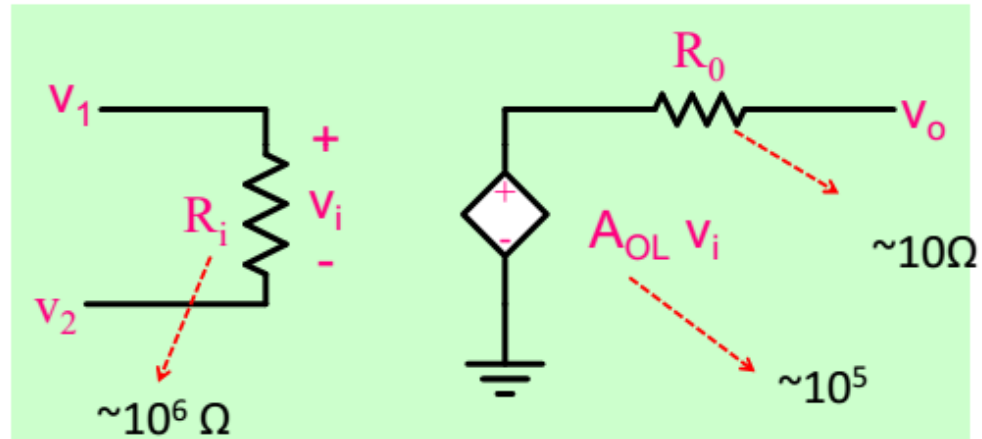
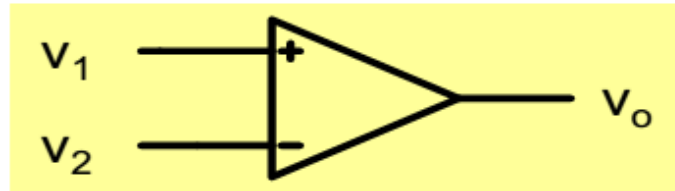


This assumes very high CMRR

Feedback

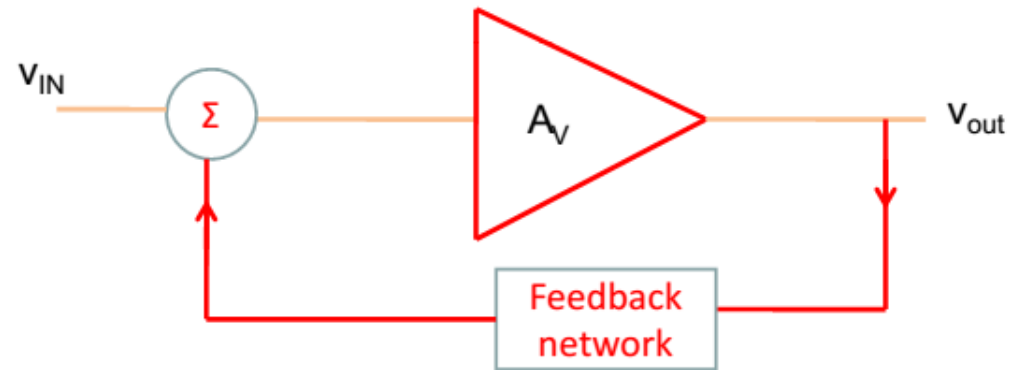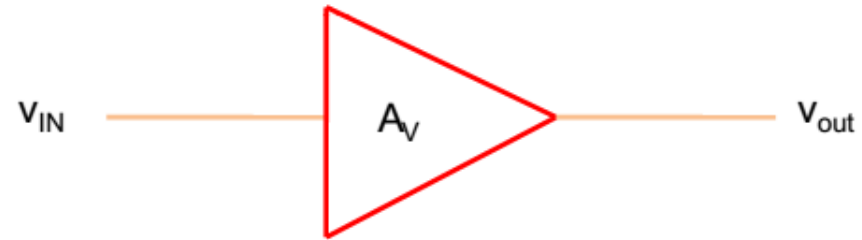


Negative and Positive Feedback

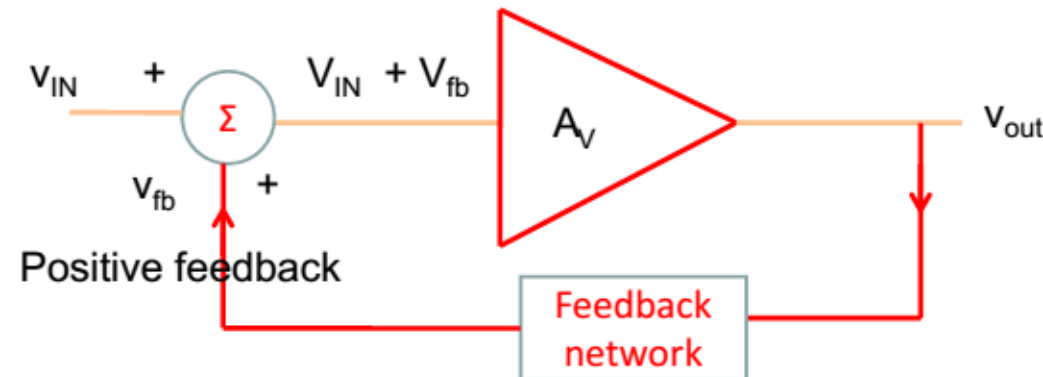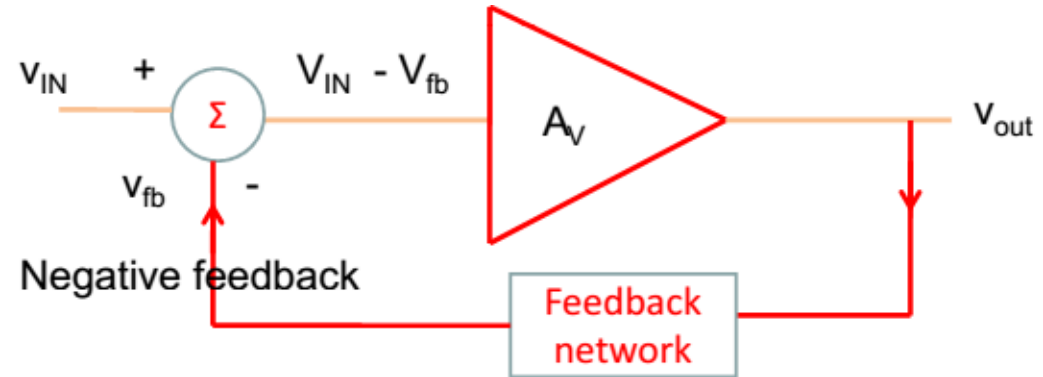


Different Op-Amp Circuits


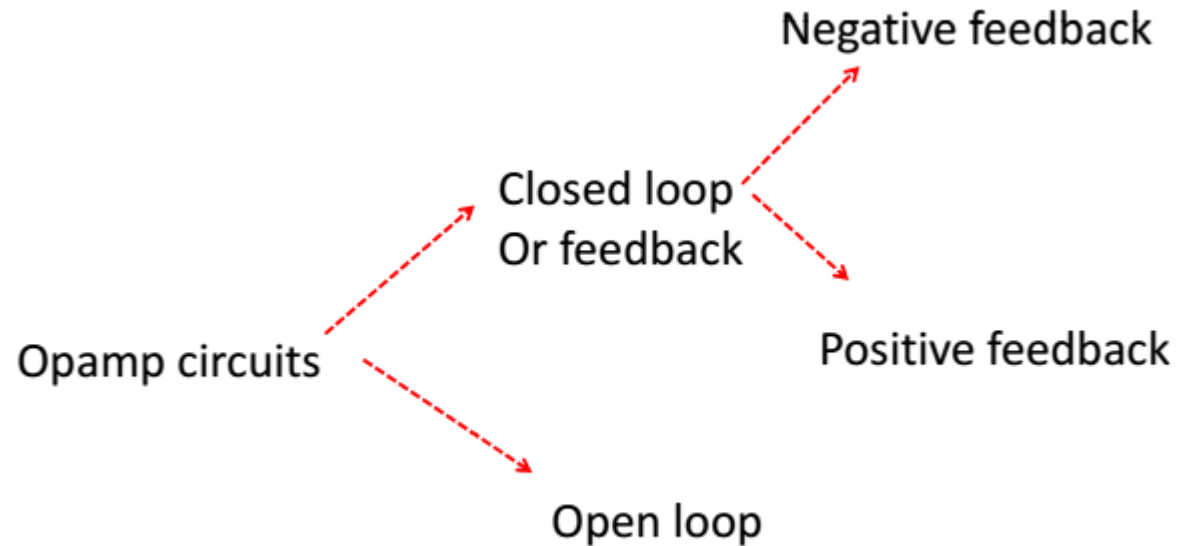
We mostly use op-amp circuits that employ negative feedback.



Op Amp with Negative Feedback

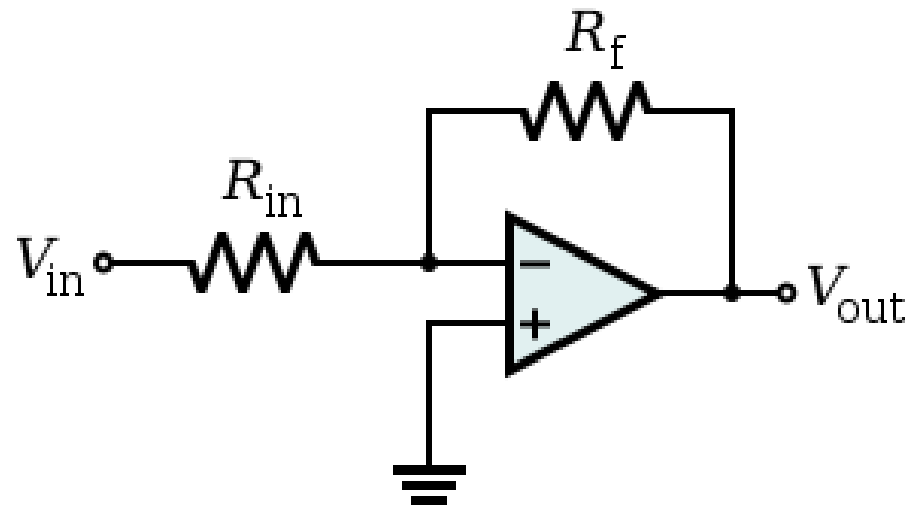


Virtual Ground Property

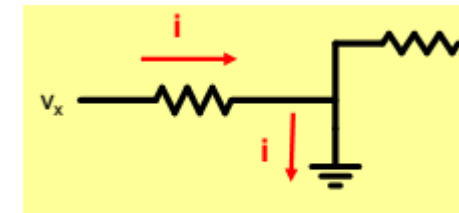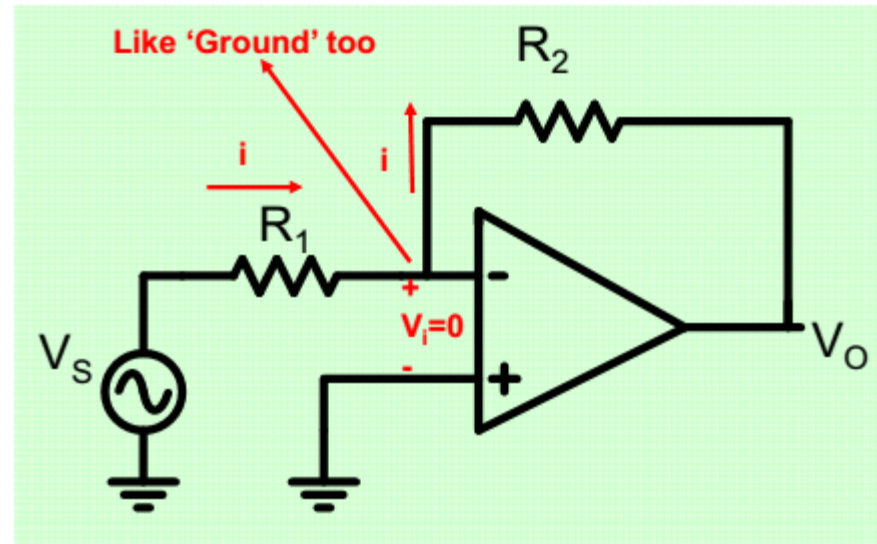

For actual ground

Virtual Ground Property

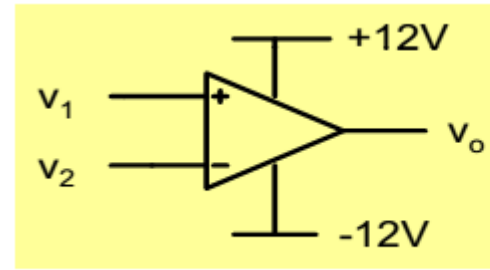

$$v_1 \cong v_2$$


In op-amp circuits employing negative feedback, the voltage at the positive input terminal is almost equal to the voltage at the negative input terminal, given that the gain of the op-amp is very high.

It does not hold under:

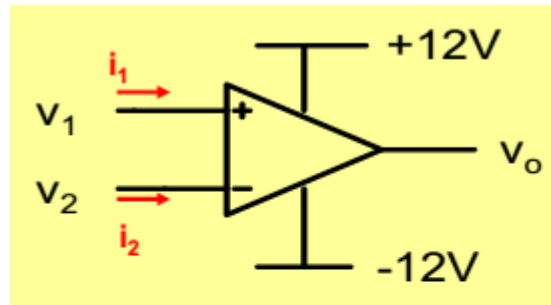1. Open Loop System
2. Positive Feedback
3. If the op-amp is saturated (that is, it is driving the maximum current that it can)

Golden Rules for Analysing Op-Amp Circuits

Note: These hold true only and only under negative feedback.




1. $v_1 = v_2$

2. $i_1 = i_2 = 0$

Some simple
amplifiers made
using Op-Amps


Inverting Amplifiers

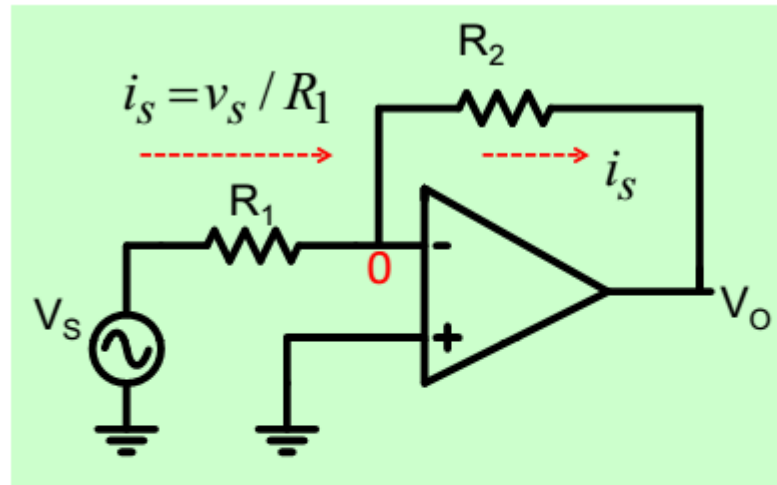

$$\frac{0 - v_o}{R_2} = i_s = \frac{v_s}{R_1}$$

$$\frac{v_o}{v_s} = -\frac{R_2}{R_1}$$

Non-Inverting Amplifiers

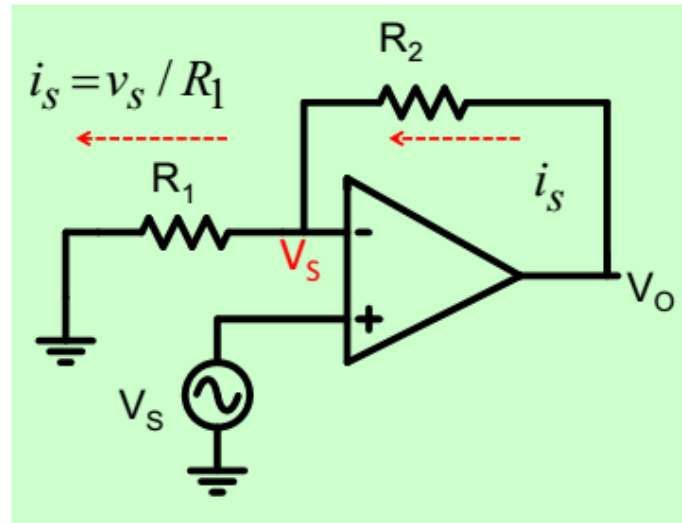

1. $v_1 = v_2$


2. $i_1 = i_2 = 0$

$$\frac{v_o - v_s}{R_2} = i_s = \frac{v_s}{R_1}$$

$$\frac{v_o}{v_s} = 1 + \frac{R_2}{R_1}$$

An Adder

Adder

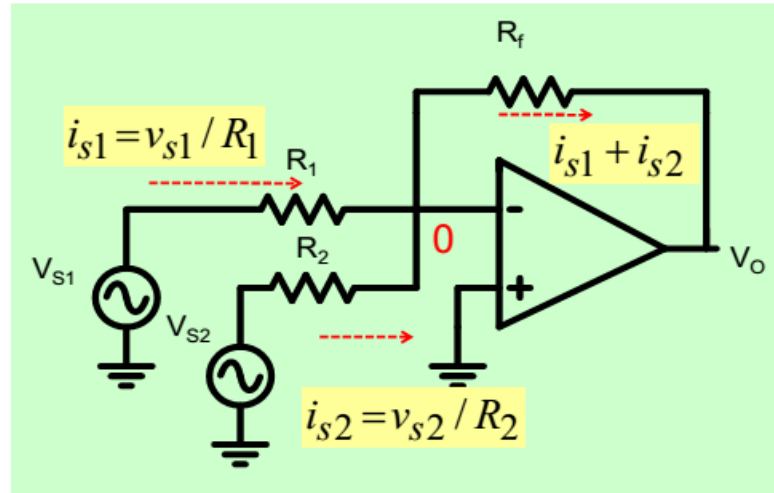


$$\frac{0 - v_o}{R_f} = i_{s1} + i_{s2} = \frac{v_{s1}}{R_1} + \frac{v_{s2}}{R_2}$$

$$v_o = -\left(\frac{R_f}{R_1}v_{s1} + \frac{R_f}{R_2}v_{s2}\right)$$

$$\text{For } R_1 = R_2 = R \quad v_o = -\frac{R_f}{R}(v_{s1} + v_{s2})$$

Integrator


Integrator

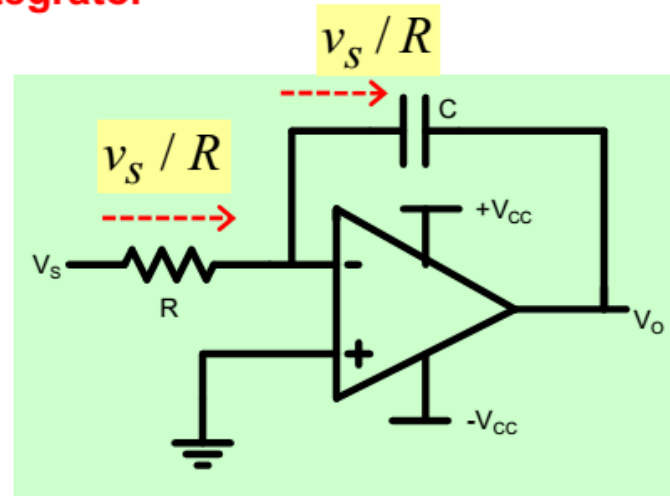

$$\frac{v_s}{R} = -C \frac{dV_o}{dt} \Rightarrow V_o(t) = -\frac{1}{RC} \int v_s dt$$


Differentiator

Differentiator

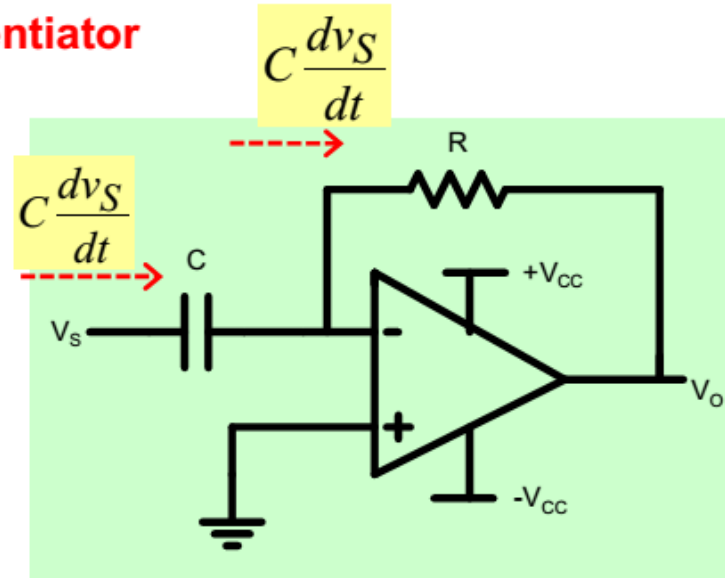

$$-\frac{V_o}{R} = C \frac{dv_s}{dt} \Rightarrow V_o(t) = -RC \frac{dv_s}{dt}$$

Instrumentation Amplifier

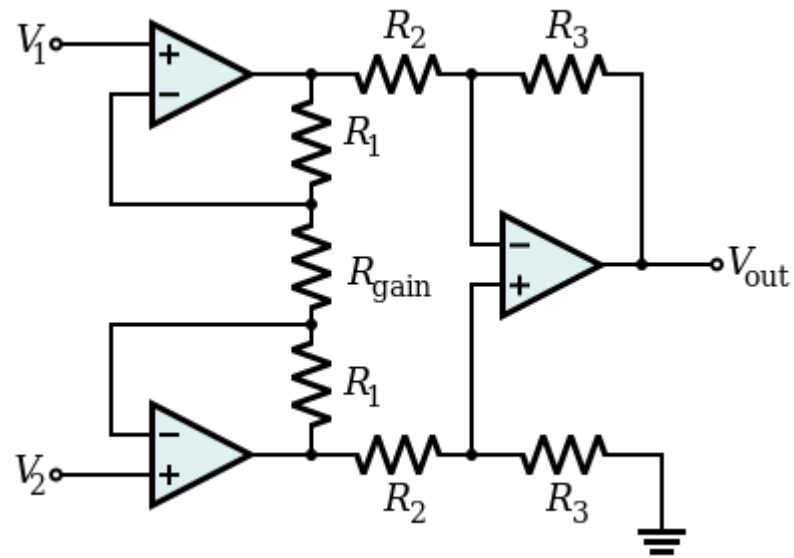

Instrumentation Amplifier


Has limited use: not as flexible as the operational amplifier
Made up for four op-amps

Feedback resistor is internal

Mainly used for high-precision gain

Only one of the resistors is determined externally that is R_g .

Analysis

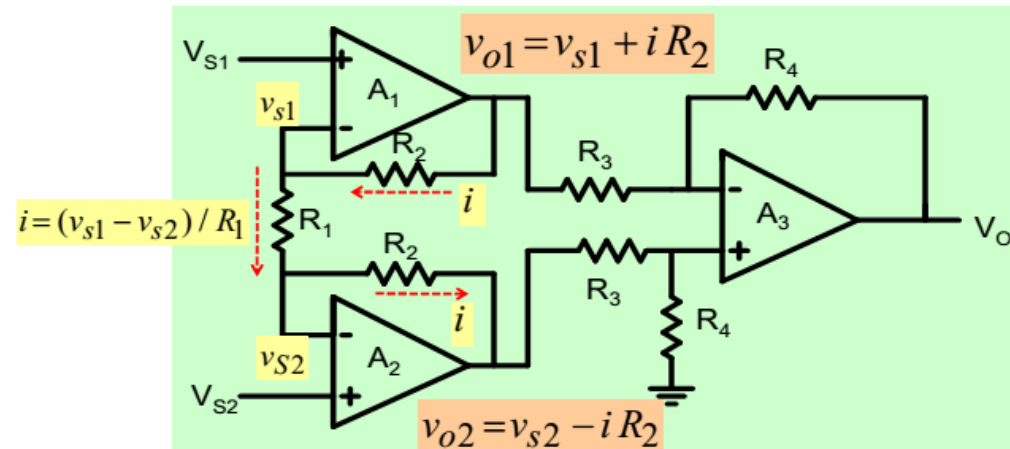

$$v_o = \frac{R_4}{R_3} \times \left(1 + \frac{2R_2}{R_1}\right) \times (v_{s2} - v_{s1})$$

Very high input Resistance

Can change one resistor R_1 and change gain

Thank You
