

Introduction to FPGA

AVI SINGH






A solid blue horizontal bar at the bottom of the slide.

Prerequisites


Digital Circuit Design - Logic Gates, FlipFlops, Counters, Mux-Demux

Familiarity with a procedural programming language like C


Logic Gates

     





Circuits using Logic Gates

 


A little more Complication

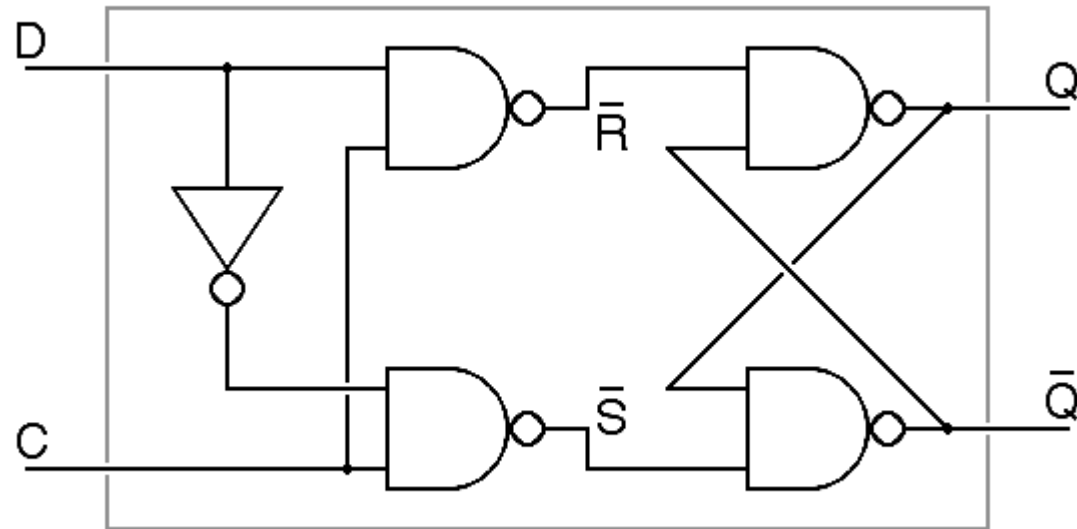

Flip Flops

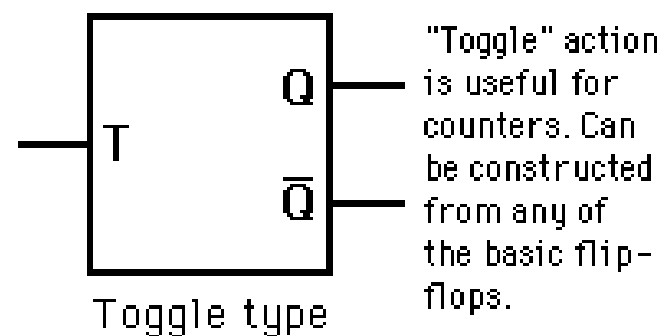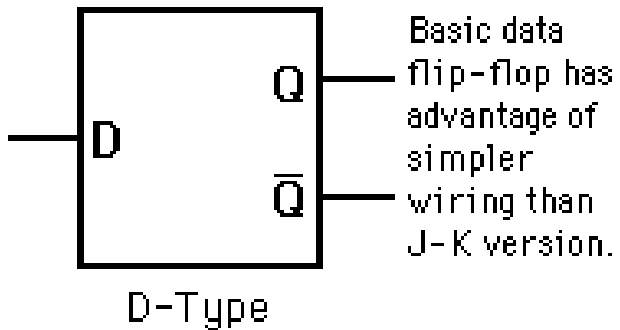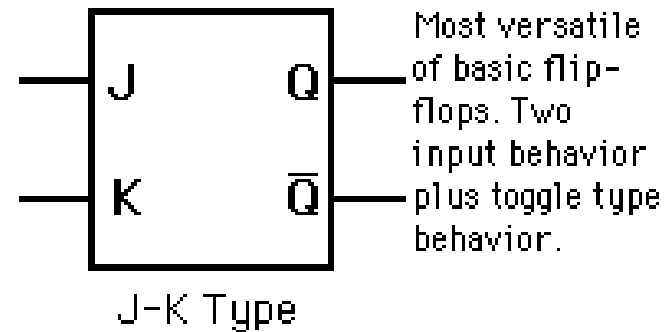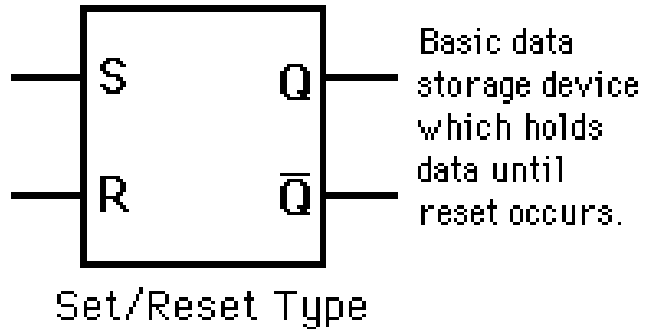

Counters

 

Microprocessors

Made up of several smaller blocks, as discussed previously.

Can contain hundreds of millions of gates.

For Example: Intel i7 ~ 731m gates!



Our Dilemma

For better performing computer, we need processors with a large number of gates.

But, how do we design with so many gates?

Do we 'draw' these circuits? Too tedious!

HDLs to the Rescue

Hardware Description Languages (HDLs)


Allow you to 'write' down hardware.

How? We will see.


Some of the popular HDLs: Verilog (mainly in the US), VHDL

 Example: A Tri-State Buffer

```
module tri_buf
(a,b,enable);
input a; output b;
input enable;
wire b;
assign b = (enable) ? a :
1'bz;
endmodule
```



How HDLs help you get the circuit

 

Where do FPGAs come in the picture?

FPGA stands for Field Programmable Gate Arrays

You can think of it as drawing board made out of silicon: you can implement any digital circuit on it.

An HDL code after synthesis can be uploaded to the FPGA, and we can test our design in the real world, before going to production with it.

How does it beat a microcontroller?


Parallel processing.

Digital Circuits are way faster than algorithms running on a CPU.

User configurable input/output pins: You can have dozens of external interrupts (or internal interrupts), have as many UART or SPI ports as you want.

You can implement a processor on an FPGA, add external memory and few other peripherals, and you have a brand new micro-controller of your own, which can even run software.

Reconfigurable Logic Blocks

 

Coding in Verilog

Consists of various building blocks called Modules

Communication between a module and its environment is achieved by using Ports

Ports are of three types: input, output, inout


Module

A “Black Box” in Verilog with inputs, outputs and internal logic working.

So, a module can be used to implement a counter.

A module is defined as `module <specific type>(<port list>);`

4029 Counter

 

One Input port for CLK

Four binary output ports

At every rising edge of clock, increment output by 1

Declaring Module

Way 1:

```
module 4029(clk, a, b, c, d, reset, enable);  
//Assuming two more input pins, reset and  
//enable with their corresponding functioning
```

Way 2:

```
module 4029(clk, out, reset, enable);
```

What is the difference in the two?

Declaring Ports

Way 1:

```
input clk;
```

```
input reset;
```

```
input enable;
```

```
output a,b,c,d;
```

Way 2:

```
input clk;
```

```
input reset;
```

```
input enable;
```

```
output [3:0] out;
```

Types of Ports

We need drivers for this module in order to interact with other modules

Driver is a way of defining something which can drive a load

Two types of drivers:

- Can store a value (for example, flip-flop)
- Cannot store a value, but connects two points (for example, a wire)

In Verilog, a driver which can store a value is called **reg** and the one which cannot is called **wire**

Drivers for 4029 modules

Ports defined as wires?

- clk
- reset
- enable

We do not need to store the values of these ports in our logical block.

Ports defined as reg?

- a,b,c,d
- out

We need to store them so that we could modify their values when required.

Defining drivers for 4029

Way 1:

```
wire clk;  
wire reset;  
wire enable;  
reg a,b,c,d;
```

Way 2:

```
wire clk;  
wire reset;  
wire enable;  
reg [3:0] out;
```

Complete definition of module

```
module 4029( clk, out, reset, enable);  
    input wire clk;  
    input wire reset;  
    input wire enable;  
    output reg [3:0] out;  
endmodule
```


Wire Vs Reg

reg can store a value, wire simply connects

Most of the times, inputs are wire and outputs are reg

Output of flip flop – wire or reg ?

Output of XOR gate – wire or reg ?

Output of multiplexer – wire or reg ?

What now?

We have seen how to define the outer structure of the modules we will use.

Time to define the internal structure and functioning?

Operational and Conditional Statements

All the arithmetic as well as logical operators in Verilog are similar to C, except ++ and -- which are not available in Verilog.

Conditional statements are also similar to C with following modifications:

- { is replaced by begin.
- } is replaced by end.

Combinatorial Circuits

Combinational circuits are acyclic interconnections of gates.

- And, Or, Not, Xor, Nand, Nor
- Multiplexers, Decoders, Encoders
- Adders, Multipliers

OUTPUT DEPENDS ON THE PRESENT INPUT ONLY.

How are these gates, muxs etc. abstracted in Verilog?

- Gates, Add, Multiply ... : by simple operators like in C
- Multiplexers ... : by control statements like if-else, case, etc.

Gate level implementation of above high level operators done by Verilog synthesizer.

Control Statements

if-else, case :

- Exactly like C.
- Hardware view: implemented using multiplexers

for loops, repeat:

- – for-loops are synthesizable only if length of iteration is determined at compile time & finite.
- repeat -similar to for loop.
- Hardware view: All loops are unrolled during synthesis.

Control Statement Syntax

```
for (i = 0; i < n; i = i + 1)
begin
    .....
end
```

```
case(address)
    0 : .....
    1 : .....
    2 : .....
    default : .....
endcase
```

```
if ( ..... )
begin
    .....
end
else begin
    .....
end
```

```
repeat (18)
begin
    .....
end
```

Assign statements

Continuous assignment statement.

Used for modeling only combinational logic.

```
module BusInverter( input wire A, output wire B );  
  assign B = ~A;  
endmodule
```

Basically B is shorted to $\sim A$.

LHS should have variable of wire type.

Example-1 bit Full Adder

GATE LEVEL DESCRIPTION

```
module full_adder(  
    input wire a,  
    input wire b,  
    input wire cin,  
    output wire sum,  
    output wire carry );  
  
    assign sum = a & ~b & ~cin | ~a & b & ~cin | ~a & ~b &  
    cin | a & b & cin;  
    assign carry = a & b | a & cin | b & cin;  
endmodule
```

BEHAVIORAL DESCRIPTION


```
module full_adder(  
    input wire a,  
    input wire b,  
    input wire cin,  
    output wire sum,  
    output wire carry );  
  
    assign { carry, sum } = a+b+cin;  
  
endmodule
```


Sequential Circuits

Circuits containing state elements are called sequential circuits

OUTPUT DEPENDS ON THE PRESENT INPUT AS WELL AS ON ITS PRESENT STATE.

 The simplest synchronous state element is the edge triggered D Flip Flop



How do you implement such an element in Verilog?

always @ block

It is an abstraction provided in Verilog to mainly implement sequential circuits.

Also used for combinational circuits.

```
always @(#sensitivity list#)
begin
    ..... //No assign statements inside always@
end
```

Execution of always block depends on the sensitivity list.

Sensitivity List

Run continuously. (mostly used in Test Benches)

```
always
```

Run when any variable changes its value.

```
always @(*) //for combinational ckts
```

Run when the variables `a' or `b' change their value.

```
always @(a, b)
```

Run when a positive edge is detected on CLK.

```
always @(posedge CLK) //for sequential ckt
```

initial block

An initial block is executed only once when simulation starts

This is useful in writing test benches

If we have multiple initial blocks, then all of them are executed at the beginning of simulation

Counter Example

```
module Counter(  
    input wire CLK,  
    output reg [3:0] OUT );  
  
    initial  
        OUT <= 0;  
  
    always @(posedge CLK)  
        OUT <= OUT + 1;  
  
endmodule
```

Blocking and Non-blocking statement

Non-blocking assignments happen in parallel.

```
always @ ( #sensitivity list # ) begin  
    B <= A ;  
    C <= B ; // (A,B) = (1,2) -> (B,C) = (1,2)  
end
```

Blocking assignments happen sequentially.

```
always @ ( #sensitivity list # ) begin  
    B = A ;  
    C = B ; // (A,B) = (1,2) -> (B,C) = (1,1)  
end
```

Points to note

Use `always@(*)` block with blocking assignments for combinational circuits.

Use `always@(posedge clk)` block with non-blocking assignments for sequential combinational circuits.

Do not mix blocking and non-blocking statements.

Complete 4029 module

```
module 4029( clk, out, reset, enable);
```

```
    input wire clk;
```

```
    input wire reset;
```

```
    input wire enable;
```

```
    output reg [3:0] out;
```

```
    always @(posedge clk)
```

```
    begin
```

```
        if (reset == 0 && enable == 0)
```

```
            begin
```

```
                out <= out +1;
```

```
            end
```

```
        end
```

```
// continued to next page
```


Complete 4029 module

```
always @(reset or enable)
begin
  if (reset == 1'b1)
  begin
    out <= 0;
  end
end

endmodule
```

How to get started?

First of all download Xilinx ISE WebPack, with a free licence.

Create a simple project, and learn to write test benches (or directly create them on the ISE), and start using the ISim tool.

Do the 'Verilog in a Day' exercises found here

<http://www.asic-world.com/>

Wire vs Reg

<http://inst.eecs.berkeley.edu/~cs150/Documents/Nets.pdf>

Check if Mojo boards are available in club.

Go here: <http://embeddedmicro.com/tutorials/mojo/>

See your code in action!

Takneek 2014

Prelims:
Objective + Subjective questions

Finals
Design problem.