

FPGA Design Challenge

Techkriti 2013

Digital Logic Design using Verilog

Part 2

By

Neeraj Kulkarni

Recap

- Verilog- Hardware Description Language
- Modules
- Combinational circuits
- assign statement
- Control statements
- Sequential circuits
- always@ block
- Blocking and non-blocking statements

Parameterized modules

- A generalized type of module.
- Can be instantiated to any value of parameter.
- Parameterization is a good practice for reusable modules
- Useful in large circuits.

Example: N-bit adder

```
module AdderN #(parameter N = 4)(  
    input wire [N-1:0] IN1,  
    input wire [N-1:0] IN2,  
    output reg [N-1:0] OUT  
);  
    always @(*)  
        OUT <= IN1 + IN2;  
endmodule
```

Modular Circuits

- Time to connect the “black boxes” together 😊
- A modular circuit is one where sub-modules are initialized with interconnects to form even a larger circuit.
- Each sub-module resides in its own Verilog file. A sub-module may use another sub-module in its circuit.

Example – Full Adder

```
module FAdder(  
    input wire [3:0] A, B,  
    output wire cout,  
    output wire [3:0] S  
);  
  
    wire c0, c1, c2;  
    FA fa0( .a(A[0]), .b(B[0]), .cin(0),.cout(c0), .sum(S[0]));  
    FA fa1( .a(A[1]), .b(B[1]), .cin(c0), .cout(c1), .sum(S[1]));  
    FA fa2( .a(A[2]), .b(B[2]), .cin(c1), .cout(c2), .sum(S[2]));  
    FA fa3( .a(A[3]), .b(B[3]), .cin(c2), .cout(cout), .sum(S[3]));  
endmodule
```

```
module FA(  
    input wire a, b, cin,  
    output wire sum,  
    output wire cout  
);  
    assign { carry, sum } = a+b +cin;  
endmodule
```

Instantiation

- **Modules:**

```
<Module Name> <Instance name>  
( .in1(...) ,  
  .in2(...),  
  .out1(...),  
  .out2(...) );
```
- **Parametrized Module:**

```
<Module Name>  
#(<Parameter Name>(value))  
<Instance name>  
( .in1(...) ,  
  .in2(...),  
  .out1(...),  
  .out2(...) );
```

Example:
AdderN #(.N(16)) Add1
(.IN1(in1) ,
 .IN2(in2),
 .OUT(out));

Points to Note

- All output ports of instantiated sub-module should be of wire data-type.
- Note in previous example, c0,c1,c2 and S are wires.
- Inputs may be reg or wire.
- Suppose in above, [3:0] S was of reg type.
 - Declare a dummy wire variable [3:0] add
 - Pass add[0], add[1] ... to the instantiations
 - Finally put:

```
always@(*)  
    S <= add;
```


Test Bench

- Used to test the functionality of design by simulation.
- Instantiate our top most module and give varying inputs & verify if the outputs match expected results.
- Added functionalities in TestBench:
 - Delays
 - \$display(), \$monitor()

Delays

- Not synthesized
 - Can be used to model delays in actual circuit during simulation
 - Used mostly in Test Benches to provide inputs at particular instants.
 - Syntax: `#<time steps>`
 - `wire #10 out; assign out = a & b;`
 - `wire out; assign #10 out = in1 & in2;`
 - `#10 q = x + y;`
 - `q = #10 x + y;`
- Most common: `always`
`#5 clk = ~clk;`

More Features

- `$display()` –
 - used for printing text or variables to screen
 - syntax is the same as for `printf` in C
 - `$display("time, \tclk, \tenable, \tcount");`
- `$monitor()` –
 - keeps track of changes to the variables in the list (`clk`, `enable`, `count`).
 - whenever any of them changes, it prints their value.
 - only written once in initial block.
 - `$monitor("%d,\t\b,\t\b,\t\b,\t%d",$time, clk, enable,count);`
- `$finish`
 - Terminating simulation

Example – Test bench Counter

```
module counter_tb;
    reg clk, reset, enable;
    wire [3:0] count;

    counter C0( .clk (clk), .reset (reset), .enable (enable), .count (count) );
    initial begin
        clk = 0;
        reset = 0;
        enable = 0;
    end
    always
        #5 clk = !clk;
    initial begin
        $display("time,\tclk,\tenable,\tcount");
        $monitor("%d,\t%b,\t%b,\t%d", $time, clk, enable, count);
    end
    initial
        #100 $finish;
endmodule
```

FPGA Design Challenge Problem Statement

Gaussian Random Number Generator

Top Module



- To construct the following module:

```
module GRNG(  
    input wire mean, var,  
    input wire enable,  
    output reg [N-1:0] random_out  
);  
    .....  
endmodule
```

- Write a Test Bench to get large number of samples from the module and write them in a file.
- Read data from file using any plotting routine (MATLAB, etc) and plot the distribution.

Some Probability theory

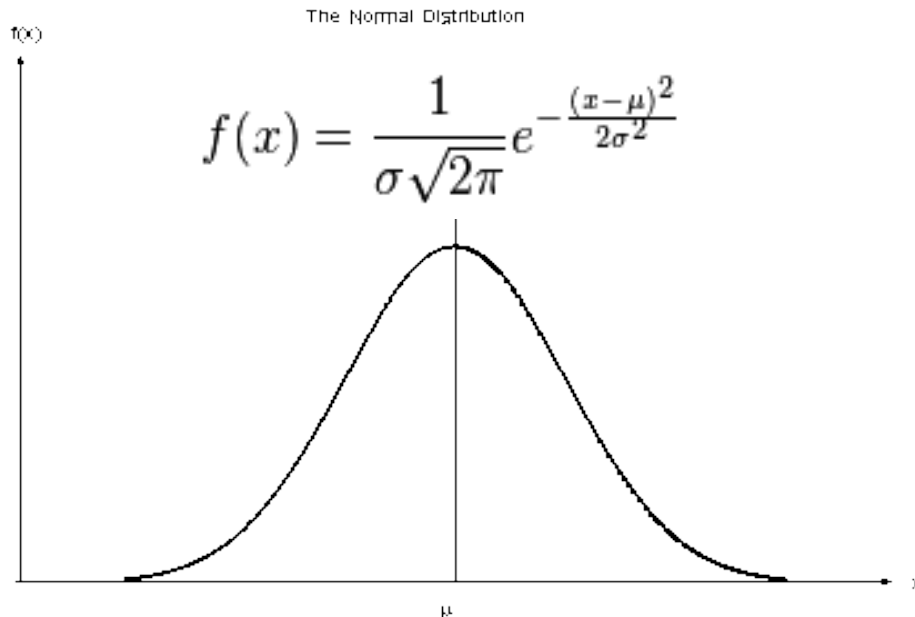 - Random Variables
 - Outcome of dice, coin
- Probability Distribution
 - Uniform distribution,
 - Gaussian Distribution



Mean: μ

Variance: Standard Deviation


$$\sigma^2 = \langle X^2 - \mu^2 \rangle$$

Central Limit Theorem

- The mean of a sufficiently large number of independent random variables, will be approximately normally distributed.
- Main principle in generating Gaussian distributed random variable.
- Suppose $\frac{X_1 + X_2 + \dots + X_N}{N} = S_N$, X_i are uniformly distributed RV with mean = μ , and variance = σ^2
- Then $\sqrt{N}(S_N - \mu) \sim N(0, \sigma^2)$.
- To convert that to a required Gaussian Distribution we can add required mean to each random number and multiply/divide by required variance to get a Gaussian distributed random numbers.

Linear Feedback Shift Registers

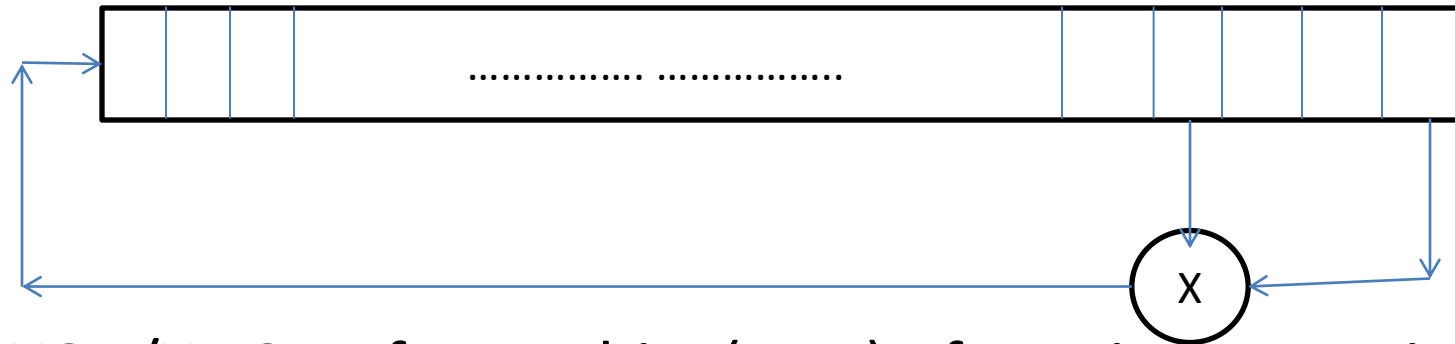- Uniform **Pseudo**-Random Number Generation



- XOR/XNOR of some bits (taps) of previous state is input bit of the shift register.
- Length of Random cycle dependent on taps.
- One with maximum cycle can be considered to fairly uniformly random.
- List of taps for given length:
http://www.xilinx.com/support/documentation/application_notes/xapp052.pdf

Note

- The approach mentioned above is one of the many possible solutions to the problem statement.
- You should search more and come up with a better solution.

Anderson-Darling Test

- The **Anderson–Darling test** is a statistical test of whether a given sample of data is drawn from a given probability distribution.
- Test for normality:

- In our case mean and variance of samples known

$$Y_i = \frac{X_i - \hat{\mu}}{\hat{\sigma}} \quad \text{where } X_i = n \text{ random samples obtained.}$$

$\mu = \text{mean}, \sigma^2 = \text{variance}$

- $$A^2 = -n - \frac{1}{n} \sum_{i=1}^n [(2i - 1) \ln \Phi(Y_i) + (2(n - i) + 1) \ln(1 - \Phi(Y_i))]$$

- Φ = standard normal cumulative distribution function.
- If $A^2 > 2.49$, implies the data is not normally distributed.
- To evaluate above, need numerical approximations of each of \ln and Φ

Extra Task

- Only if you complete the compulsory task
- Write an encoder and decoder for LDPC codes.
- Add the GRN (Noise) to output of encoder and pass it as input to decoder.
- Do it for large number samples, and get number of errors.
- Repeat for different values of SNR and plot the BER curve for the system.

Questions?